



### PART LIST

- 1 XFORMER 2X6V, 3VAC
- 1 REGULATOR LM7806
- 1 REGULATOR LM7906
- 2 CAPACITORS 100NF
- 2 CAPACITORS 1000 µF 16V
- 4 DIODES 1N4001
- 2 HEAT DISSIPATORS

WARNING: THE XFORMER SIZE MAY VARY  
FROM A BRAND TO ANOTHER :  
ADAPT THE LAYOUT TO THE ACTUAL  
XFORMER PINS SPACING

TO BE PRINTED AT SCALE 1:0  
FOR PHOTO-ETCHING  
OR TO BE COPIED AT SCALE 1:0  
FOR TRADITIONAL MANUAL PROCESS

THIS POWER-SUPPLY WILL WORK  
WITH ANY ROCKMAN HEADPHONE AMP,  
PROVIDED IT HAS THE PROPER TRS MINI-JACK  
ON THE SIDE OF THE ENCLOSURE

TRS WIRING IS:

- T = +6V
- R = -6V
- S = GROUND

JARK - BORDEAUX, FRANCE - 2006  
MAJA33@WANADOO.FR